

**ELEC-374 Digital Systems Engineering
Laboratory Project**

Winter 2021

Designing a Simple RISC Computer: Phase 1

1. Objectives

The purpose of this project is to design, simulate, implement, and verify a simple RISC Computer (Mini SRC) consisting of a simple RISC processor, memory, and I/O. Phase 1 of this project consists of the design and Functional Simulation of a part of the Mini SRC datapath. The complete datapath is shown in Section 2. In this Phase, you will design the necessary logic and simulate the *add*, *sub*, *mul*, *div*, *and*, *or*, *shr*, *shl*, *ror*, *rol*, *neg*, and *not* instructions. Note that the “Select and Encode” logic, “CON FF” Logic, “Input/Output” ports, “Memory Subsystem” and load/store instructions, branch and jump instructions, as well as *addi*, *andi*, and *ori* instructions will be designed and simulated in Phase 2.

Design input can be done using an all HDL, or a mixed schematic/HDL approach. You may use components such as gates, registers, buffers, multiplexers, encoders, etc., available in the Quartus II Library, which can be configured using the Wizard facility. You may use such components for some part of your ALU, but you must have your own advanced multiplication circuitry ([32x32 Booth algorithm with bit-pair recoding of multiplier](#)). Note that you are not allowed to use simple arithmetic operators in HDL languages for the ALU implementation of this project, such as the adder or subtractor circuitry. However, you may use + or – arithmetic operators in the implementation of your multiplier, or your divider if you opt to, as the intention here is on the implementation of a particular algorithm discussed in class for multiplication/division.

2. Preliminaries

2.1 DataPath: Figure 1 illustrates a simplified single-bus Datapath for the Mini SRC (see Figure 4.2 on page 143 and Figure 4.3 on page 148 of the Lab Reader). As shown in Figure 1, the datapath consists of a 32-bit bus, BUS. The bus is responsible for transferring the information among different components of the system. There can be only one transaction at a time on a single bus. There are sixteen 32-bit registers *R0* through *R15* in the Mini SRC, as discussed in the CPU specification. There are also two dedicated 32-bit registers *HI* and *LO* for holding the result of a multiplication or a division operation. The 32-bit *Instruction Register*, *IR*, holds the current instruction. The 32-bit *Program Counter*, *PC*, points to the address of the next instruction after the execution of the current instruction. *PC* is incremented by 1 during the instruction fetch, using *IncPC* control signal in the *Arithmetic Logic Unit* (ALU). You may instead opt for a hardware incrementer outside ALU. In general, you are welcome to come up with your own ideas and design decisions during the entire CPU design project.

The ALU has two inputs, A and B, and an output, C. Because the bus can support only one transaction at a time, one of the inputs (A input) to the ALU needs to be stored in the 32-bit temporary register, Y. As discussed in the [CPU Specification document](#), the ALU supports the addition, subtraction, multiplication, division, shift right, shift left, rotate right, rotate left, logical AND, Logical OR, negate, and NOT operations. The control signals to the ALU (generated by the Control Unit in Phase 3, as shown in Figure 5) will enforce the required operation. These control signals include *ADD*, *SUB*, *MUL*, *DIV*, *SHR*, *SHL*, *ROR*, *ROL*, *AND*, *OR*, *NEG*, and *NOT* control signals, among others. Note that in Phase 1 and Phase 2, you simulate such control

signals. The Z register holds the result of the operation in ALU and will be able to drive the Bus in the next clock cycle when the bus is free. The Z register is 64-bit long to hold the result of a multiplication (product) or a division (remainder in the higher byte, and quotient in the lower byte) operation temporarily before loading the *HI* and *LO* registers. You may need a multiplexer between the Y register and the A input of the ALU for any other potential input. You may also need to include a simple circuitry (such as a multiplexer) between the ALU output C and the Z register. Depending on the current instruction in the Instruction Register, *IR*, this logic selects the output of one of the ALU units to drive the Z register.

The *Memory Address register (MAR)* holds the address of a memory location. The *Memory Data Register (MDR)* holds either the data read from memory, or the data to be written into the memory. The *Select and Encode Logic* signals allow transfer of the contents of a register onto the bus, as well as loading the registers with the contents of the bus. The *CON FF Logic* is used to determine if the condition is met to allow branching to take place. The *Input (In.Port)* and *Output (Out.Port)* registers are 32-bit registers each, and are used to connect the CPU to the outside world.

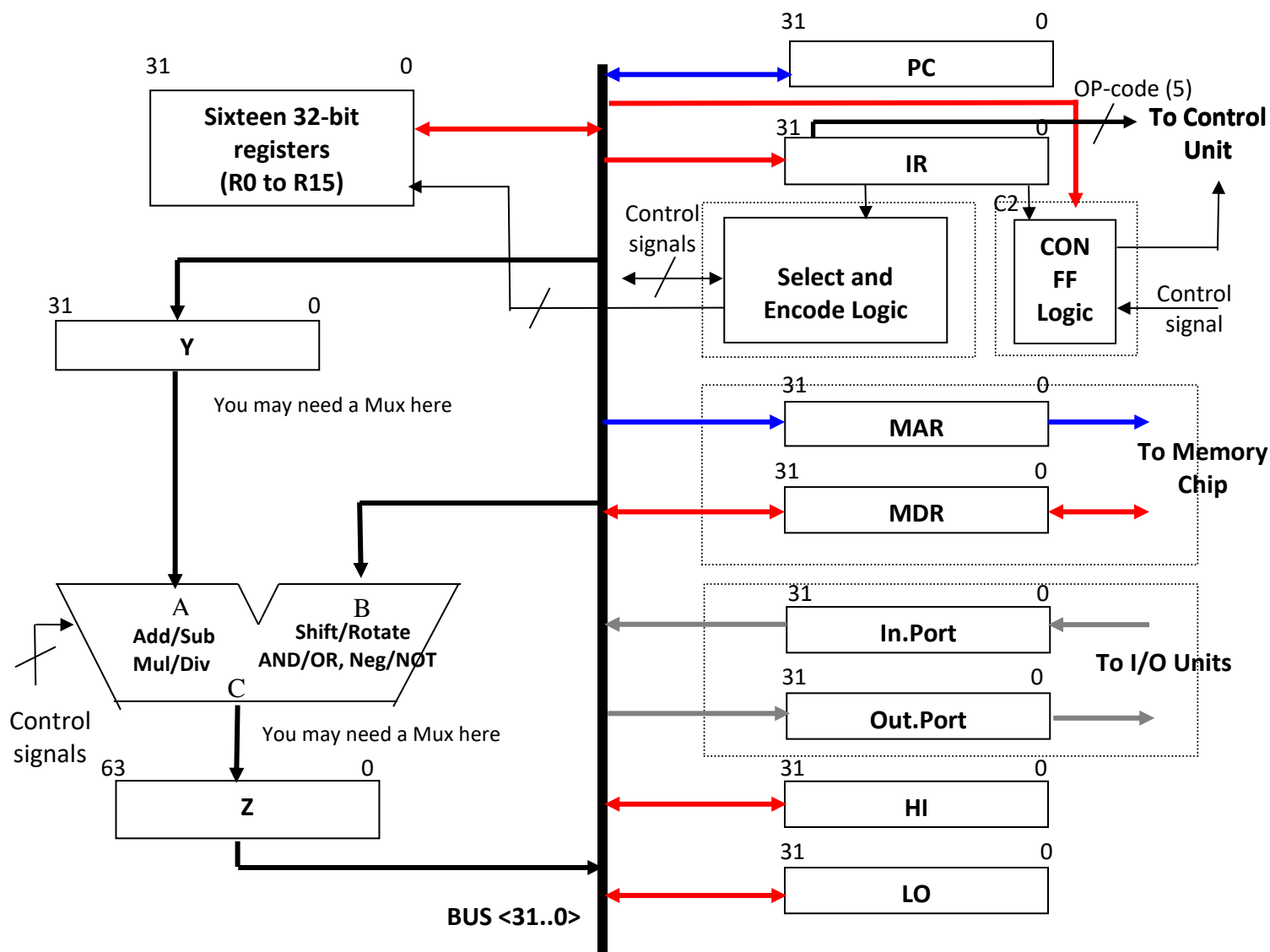


Figure 1: Simplified datapath

As a reminder, the “Select and Encode logic”, “CON FF Logic”, “Input/Output ports”, “Memory Subsystem” and load/store instructions, branch and jump instructions, as well as *addi*, *andi*, and *ori* instructions will be tackled in Phase 2. The information provided here is for the sake of the completeness in describing the datapath. More information about these units will be provided in Phase 2.

A Typical Register: Figure 2 shows the block diagram for a typical register, such as *R1* (there will be a minor revision to *R0* circuitry that we will discuss in Phase 2 when we design the “Select and Encode Logic”). The input to the register, **BusMuxOut**, is coming directly from the bus. The contents of the bus is saved onto the register using the synchronous *Clock* signal and the *R1in* signal. The *R1in* signal is the control signal that allows the data from the bus to be written onto the register *R1*. The *R1out* signal is the control signal that allows the contents of *R1* to be placed on the bus, through the **BusMuxIn-R1** input (see Figure 3). The *Clear* signal is used to reset the registers to a known state.

 


Figure 2: A typical register

Bus design: One of the important aspects of the Mini SRC datapath is its bus. The Bus may be implemented by tri-state buffers, or by a multiplexer and an encoder. Figure 3 shows a typical bus design using the multiplexer/encoder approach. The Mini SRC Bus is implemented using a 32:1 Multiplexer, **BusMux**, with five select input signals coming from a 32-to-5 encoder. The idea is to choose only one of the registers *R0* to *R15*, *HI*, *LO*, *Z_{high}*, *Z_{low}*, *PC*, *MDR*, *In.Port*, or the sign-extended version of the constant *C*, as the source of the bus. The output of the BusMux, **BusMuxOut**, is the Bus itself. The inputs to the 32-to-5 encoder, which could select any of the above registers, are the control signals generated by the Control Unit (in Phase 3) or by the “Select and Encode Logic” (in Phase 2). However, in Phase 1, we just simulate these signals.

 


Figure 3: A typical Bus

Memory Data Register: The *Memory Data Register (MDR)* is different from the other registers in the sense that it has two input sources and two output sources. Figure 4 presents how *MDR* is connected to the memory bus, and to the internal bus. The inputs to the *MDR* comes from the memory unit (**Mdatain**) or from the Bus (**BusMuxOut**). Data is stored in the *MDR* using the synchronous *Clock* signal and the *MDRin* control signal. The *MDR* contents can be written into the memory or drive the Bus.

 


Figure 4: The MDR unit

2.2 Control Unit: The Control unit is to be designed in Phase 3. However, a block diagram is provided in Figure 5 for a better understanding of the Datapath. The Control Unit is at the heart of the processor. It accepts as inputs those signals that are needed to operate the processor and provides as outputs all the control signals necessary to execute the instructions. The outputs from the Control Unit are the control signals that we use to generate **Control Sequences** for the instructions of the Mini SRC.

Please note that you should not be concerned about the instruction decoding in Phase 1 and Phase 2 of this project. Instruction decoding will be done in Phase3 with VHDL or Verilog. The details of the Control Unit will be discussed in Phase 3.

 


Figure 5: Block diagram of the Control Unit

3. Lab Procedure and Report

Design the datapath shown in Figure 1 (except for the “Select and Encode Logic”, “CON FF Logic”, “Memory chip in the Memory Subsystem”, and “Input/Output ports” units) using an all HDL (VHDL or Verilog) or a mixed schematic/HDL in Quartus II design software. You are advised to follow the steps below when designing your datapath:

1. Design the registers R0 to R15, PC, IR, Y, Z, MAR, HI, and LO (see Figures 1 and 2).
2. Design the bidirectional Bus (Figure 3) and connect the registers that you designed in Step 1 to the Bus.
3. Design the MDR unit (Figure 4) and connect it to the BUS. Leave the rest of the Memory Subsystem (connection to the memory chip) for Phase 2.
4. Design your ALU. Start with simple ALU operations such as logical AND, etc. Then, design the more involved operations such as ADD/SUB, MUL, and DIV circuitry. Finally, design the rest of the ALU operations.
 - For the multiplication unit, you are to design your own [32x32 Booth algorithm with bit-pair recoding of multiplier](#).
 - During the term, you may design and implement any other advanced design techniques that you learned in class for a bonus marks.

You are advised to functionally simulate your design as you go through different design steps. In order to test the Datapath by Functional Simulation, the following control and output signals may be required. In Phase 3, these control signals will be generated by the Control Unit.

Control Signals: R0in, R0out; R1in, R1out; ...; R15in, R15out; Hlin; Hlout; LOin; LOout; PCin, PCout; IRin; Zin; Zhighout, Zlowout; Yin; MARin; MDRin, MDRout; Read; Mdatain[31..0]

Outputs: R0, R1, ..., R15, HI, LO, IR, BusMuxOut, Z (minimum required output signals for demo to TA in lab), and any other outputs you may wish to observe in your simulation.

Using the following control sequences, test your design for *and*, *or*, *add*, *sub*, *mul*, *div*, *shr*, *shl*, *ror*, *rol*, *neg*, and *not* instructions.

3.a) In your reports, demonstrate that your Logical AND circuitry works correctly by simulating the Control Sequence for the logical ***and R5, R2, R4*** instruction (similar to table 4.7 on page 155 of the Lab Reader for the “add” instruction), modified for the Datapath in isolation, as follows:

Control Sequence:

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, Yin
T4	R4out, AND, Zin
T5	Zlowout, R5in

Notes: T0 , T1, and T2 steps are used for the instruction fetch.

In T1, Mdatain[31..0] should be set to the 32-bit pattern for the *and R5, R2, R4* instruction. Its pattern can be determined by referring to the specification of Mini SRC.

In Phase 2, the opcode will directly come from the memory chip, but note that you may need to insert a control signal to make sure when your memory data becomes available.

Do not consider instruction decoding for Phase 1 and Phase 2. It will be done in Phase 3.

As demonstrated in the tutorial on Quartus II and ModelSim-Altera, to simulate your design using ModelSim, you will need to write a testbench program in VHDL or Verilog. Here is a sample testbench template in VHDL for the logical AND instruction, ***and R5, R2, R4***, which you may need to verify and revise for other instructions.

-- and datapath_tb.vhd file: <This is the filename>

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

-- entity declaration only; no definition here

```
ENTITY datapath_tb IS  
END ENTITY datapath_tb;
```

-- Architecture of the testbench with the signal names

ARCHITECTURE datapath_tb_arch OF datapath_tb IS -- Add any other signals to see in your simulation

```
SIGNAL      PCout_tb, Zlowout_tb, MDRout_tb, R2out_tb, R4out_tb:      std_logic;  
SIGNAL      MARin_tb, Zin_tb, PCin_tb, MDRin_tb, IRin_tb, Yin_tb:    std_logic;  
SIGNAL      IncPC_tb, Read_tb, AND_tb, R5in_tb, R2in_tb, R4in_tb:    std_logic;  
SIGNAL      Clock_tb:                                              std_logic;  
SIGNAL      Mdatain_tb      :                                       std_logic_vector (31 downto 0);  
  
TYPE        State IS (default, Reg_load1a, Reg_load1b, Reg_load2a, Reg_load2b, Reg_load3a, Reg_load3b, T0, T1,  
                      T2, T3, T4, T5);  
SIGNAL      Present_state: State := default;
```

-- component instantiation of the datapath

```
COMPONENT datapath  
PORT (  
    PCout, Zlowout, MDRout, R2out, R4out:      in      std_logic;  
    MARin, Zin, PCin, MDRin, IRin, Yin:        in      std_logic;  
    IncPC, Read, AND, R5in, R2in, R4in:        in      std_logic;  
    Clock:                                     in      Std_logic;  
    Mdatain:                                  in      std_logic_vector (31 downto 0);  
END COMPONENT datapath;
```

BEGIN

DUT : datapath

--port mapping: between the dut and the testbench signals

```
PORT MAP (  
    PCout      =>    PCout_tb,  
    Zlowout    =>    Zlowout_tb,  
    MDRout     =>    MDRout_tb,  
    R2out      =>    R2out_tb,  
    R4out      =>    R4out_tb,  
    MARin      =>    MARin_tb,  
    Zin        =>    Zin_tb,  
    PCin       =>    PCin_tb,  
    MDRin      =>    MDRin_tb,  
    IRin       =>    IRin_tb,  
    Yin        =>    Yin_tb,  
    IncPC      =>    IncPC_tb,  
    Read       =>    Read_tb,  
    AND        =>    AND_tb,
```



```

R2in      =>    R2in_tb,
R4in      =>    R4in_tb,
R5in      =>    R5in_tb,
Clock     =>    Clock_tb,
Mdatain   =>    Mdatain_tb);

```

--add test logic here

```

Clock_process: PROCESS IS

```

```

BEGIN

```

```

    Clock_tb <= '1', '0' after 10 ns;

```

```

    Wait for 20 ns;

```

```

END PROCESS Clock_process;

```

```

PROCESS (Clock_tb) IS      -- finite state machine

```

```

BEGIN

```

```

    IF (rising_edge (Clock_tb)) THEN

```

-- if clock rising-edge

```

        CASE Present_state IS

```

```

            WHEN Default =>

```

```

                Present_state <= Reg_load1a;

```

```

            WHEN Reg_load1a =>

```

```

                Present_state <= Reg_load1b;

```

```

            WHEN Reg_load1b =>

```

```

                Present_state <= Reg_load2a;

```

```

            WHEN Reg_load2a =>

```

```

                Present_state <= Reg_load2b;

```

```

            WHEN Reg_load2b =>

```

```

                Present_state <= Reg_load3a;

```

```

            WHEN Reg_load3a =>

```

```

                Present_state <= Reg_load3b;

```

```

            WHEN Reg_load3b =>

```

```

                Present_state <= T0;

```

```

            WHEN T0 =>

```

```

                Present_state <= T1;

```

```

            WHEN T1 =>

```

```

                Present_state <= T2;

```

```

            WHEN T2 =>

```

```

                Present_state <= T3;

```

```

            WHEN T3 =>

```

```

                Present_state <= T4;

```

```

            WHEN T4 =>

```

```

                Present_state <= T5;

```

```

            WHEN OTHERS =>

```

```

        END CASE;

```

```

    END IF;

```

```

END PROCESS;

```

```

PROCESS (Present_state) IS      -- do the required job in each state

```

BEGIN

CASE Present_state IS -- assert the required signals in each clock cycle

WHEN Default =>

PCout_tb <= '0'; Zlowout_tb <= '0'; MDRout_tb <= '0'; -- initialize the signals
R2out_tb <= '0'; R4out_tb <= '0'; MARin_tb <= '0'; Zin_tb <= '0';
PCin_tb <= '0'; MDRin_tb <= '0'; IRin_tb <= '0'; Yin_tb <= '0';
IncPC_tb <= '0'; Read_tb <= '0'; AND_tb <= '0';
R2in_tb <= '0'; R4in_tb <= '0'; R5in_tb <= '0'; Mdatain_tb <= x"00000000";

WHEN Reg_load1a =>

Mdatain_tb <= x"00000022";
Read_tb <= '0', '1' after 10 ns, '0' after 25 ns; -- the first zero is there for completeness
MDRin_tb <= '0', '1' after 10 ns, '0' after 25 ns;

WHEN Reg_load1b =>

MDRout_tb <= '1' after 10 ns, '0' after 25 ns;
R2in_tb <= '1' after 10 ns, '0' after 25 ns; -- initialize R2 with the value \$22

WHEN Reg_load2a =>

Mdatain_tb <= x"00000024";
Read_tb <= '1' after 10 ns, '0' after 25 ns;
MDRin_tb <= '1' after 10 ns, '0' after 25 ns;

WHEN Reg_load2b =>

MDRout_tb <= '1' after 10 ns, '0' after 25 ns;
R4in_tb <= '1' after 10 ns, '0' after 25 ns; -- initialize R4 with the value \$24

WHEN Reg_load3a =>

Mdatain_tb <= x"00000026";
Read_tb <= '1' after 10 ns, '0' after 25 ns;
MDRin_tb <= '1' after 10 ns, '0' after 25 ns;

WHEN Reg_load3b =>

MDRout_tb <= '1' after 10 ns, '0' after 25 ns;
R5in_tb <= '1' after 10 ns, '0' after 25 ns; -- initialize R5 with the value \$26

WHEN T0 =>

-- see if you need to de-assert these signals

PCout_tb <= '1'; MARin_tb <= '1'; IncPC_tb <= '1'; Zin_tb <= '1';

WHEN T1 =>

Zlowout_tb <= '1'; PCin_tb <= '1'; Read_tb <= '1'; MDRin_tb <= '1';
Mdatain_tb <= x"4A920000"; -- opcode for "and R5, R2, R4"

WHEN T2 =>

MDRout_tb <= '1'; IRin_tb <= '1';

WHEN T3 =>

R2out_tb <= '1'; Yin_tb <= '1';

WHEN T4 =>

R4out_tb <= '1'; AND_tb <= '1'; Zin_tb <= '1';

WHEN T5 =>

Zlowout_tb <= '1'; R5in_tb <= '1';

WHEN OTHERS =>

END CASE;

END PROCESS;

END ARCHITECTURE datapath_tb_arch;

Here is a sample testbench template in Verilog for the logical AND instruction, *and R5, R2, R4*, which you may need to verify and revise for other instructions.

```
// and datapath_tb.v file: <This is the filename>
`timescale 1ns/10ps
module datapath_tb;
    reg  PCout, Zlowout, MDRout, R2out, R4out;    // add any other signals to see in your simulation
    reg  MARin, Zin, PCin, MDRin, IRin, Yin;
    reg  IncPC, Read, AND, R5in, R2in, R4in;
    reg  Clock;
    reg  [31:0] Mdatain;

    parameter  Default = 4'b0000, Reg_load1a = 4'b0001, Reg_load1b = 4'b0010, Reg_load2a = 4'b0011,
               Reg_load2b = 4'b0100, Reg_load3a = 4'b0101, Reg_load3b = 4'b0110, T0 = 4'b0111,
               T1 = 4'b1000, T2 = 4'b1001, T3 = 4'b1010, T4 = 4'b1011, T5 = 4'b1100;
    reg  [3:0] Present_state = Default;

    Datapath DUT(PCout, Zlowout, MDRout, R2out, R4out, MARin, Zin, PCin, MDRin, IRin, Yin, IncPC, Read, AND, R5in,
    R2in, R4in, Clock, Mdatain);

    // add test logic here
    initial
        begin
            Clock = 0;
            forever #10 Clock = ~ Clock;
        end

    always @(posedge Clock)    // finite state machine; if clock rising-edge
        begin
            case (Present_state)    // #40 was added in week 5, this will cover later time delays
                Default            :    #40    Present_state = Reg_load1a;
                Reg_load1a         :    #40    Present_state = Reg_load1b;
                Reg_load1b         :    #40    Present_state = Reg_load2a;
                Reg_load2a         :    #40    Present_state = Reg_load2b;
                Reg_load2b         :    #40    Present_state = Reg_load3a;
                Reg_load3a         :    #40    Present_state = Reg_load3b;
                Reg_load3b         :    #40    Present_state = T0;
                T0                 :    #40    Present_state = T1;
                T1                 :    #40    Present_state = T2;
                T2                 :    #40    Present_state = T3;
                T3                 :    #40    Present_state = T4;
                T4                 :    #40    Present_state = T5;

            endcase
        end

    always @(Present_state)    // do the required job in each state
```

```

begin
case (Present_state)           // assert the required signals in each clock cycle
  Default: begin
    PCout <= 0; Zlowout <= 0; MDRout <= 0;           // initialize the signals
    R2out <= 0; R4out <= 0; MARin <= 0; Zin <= 0;
    PCin <= 0; MDRin <= 0; IRin <= 0; Yin <= 0;
    IncPC <= 0; Read <= 0; AND <= 0;
    R5in <= 0; R2in <= 0; R4in <= 0; Mdatain <= 32'h00000000;

  end
  Reg_load1a: begin
    Mdatain <= 32'h00000022;
    Read = 0; MDRin = 0;           // the first zero is there for completeness
    #10 Read <= 1; MDRin <= 1;
    #15 Read <= 0; MDRin <= 0;

  end
  Reg_load1b: begin
    #10 MDRout <= 1; R2in <= 1;
    #15 MDRout <= 0; R2in <= 0;   // initialize R2 with the value $22

  end
  Reg_load2a: begin
    Mdatain <= 32'h00000024;
    #10 Read <= 1; MDRin <= 1;
    #15 Read <= 0; MDRin <= 0;

  end
  Reg_load2b: begin
    #10 MDRout <= 1; R4in <= 1;
    #15 MDRout <= 0; R4in <= 0;   // initialize R4 with the value $24

  end
  Reg_load3a: begin
    Mdatain <= 32'h00000026;
    #10 Read <= 1; MDRin <= 1;
    #15 Read <= 0; MDRin <= 0;

  end
  Reg_load3b: begin
    #10 MDRout <= 1; R5in <= 1;
    #15 MDRout <= 0; R5in <= 0;   // initialize R5 with the value $26

  end

  T0: begin           // see if you need to de-assert these signals
    PCout <= 1; MARin <= 1; IncPC <= 1; Zin <= 1;

  end
  T1: begin
    Zlowout <= 1; PCin <= 1; Read <= 1; MDRin <= 1;
    Mdatain <= 32'h4A920000;           // opcode for "and R5, R2, R4"

  end
  T2: begin
    MDRout <= 1; IRin <= 1;

  end
end

```

```

T3: begin
    R2out <= 1; Yin <= 1;
end
T4: begin
    R4out <= 1; AND <= 1; Zin <= 1;
end
T5: begin
    Zlowout <= 1; R5in <= 1;
end
endcase
end
endmodule

```

3.b) Demonstrate that your Logical OR design works fine by simulating the Control Sequence for the **or R5, R2, R4** instruction. The Control Sequence is the same as the one for the *and* instruction except for using the OR control signal in T4 instead of the AND signal.

3.c) Demonstrate that your Adder works correctly by simulating the Control Sequence for the **add R5, R2, R4** instruction, modified for the Datapath in isolation, as follows:

Control Sequence:

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, Yin
T4	R4out, ADD, Zin
T5	Zlowout, R5in

3.d) Demonstrate that your Subtractor circuitry works fine by simulating the Control Sequence for the **sub R5, R2, R4** instruction. The Control Sequence is the same as the one used for the *add* instruction except for using the SUB control signal in T4 instead of the ADD signal.

3.e) Demonstrate that your Multiplication circuitry works correctly by simulating the Control Sequence for the **mul R2, R4** instruction.

Control Sequence:

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, Yin
T4	R4out, MUL, Zin
T5	Zlowout, LOin
T6	Zhighout, Hlin

You may need to use control signals to wait for the completion of the multiplication operation.

3.f) Demonstrate that your Division circuitry works fine by simulating the Control Sequence for the **div R2, R4** instruction. The Control Sequence is similar to the *mul* instruction except for using the DIV control signal in T4 instead of the MUL signal. Be careful where the quotient and remainder are loaded inside the Z register, and change T5 and T6 control signals accordingly.

3.g) Demonstrate that your Shift Right circuitry works correctly by simulating the Control Sequence for the **shr R5, R2, R4** instruction. The following Control Sequence is for a one-time shift right operation. Revise it accordingly for the count in R4.

Control Sequence:

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, Yin
T4	SHR, Zin
T5	Zlowout, R5in

3.h) Demonstrate that your Shift Left circuitry works fine by simulating the Control Sequence for the **shl R5, R2, R4** instruction. The Control Sequence is the same as the *shr* instruction except for using the SHL control signal in T4 instead of SHR.

3.i) Demonstrate that your Rotate Right circuitry works fine by simulating the Control Sequence for the **ror R5, R2, R4** instruction. The following Control Sequence is for a one-time rotate right operation. Revise it accordingly for the count in R4.

Control Sequence:

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, Yin
T4	ROR, Zin
T5	Zlowout, R5in

3.j) Demonstrate that your Rotate left circuitry works correctly by simulating the Control Sequence for the **rol R5, R2, R4** instruction. The Control Sequence is the same as the *ror* instruction except for using the ROL control signal in T4 instead of ROR.

3.k) Demonstrate that your Negate circuitry works correctly by simulating the Control Sequence for the **neg R5, R2** instruction.

Control Sequence:

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, NEG, Zin
T4	Zlowout, R5in

3.l) Demonstrate that your NOT circuitry works correctly by simulating the Control Sequence for the **not R5, R2** instruction. The Control Sequence is the same as the *neg* instruction except for using the NOT control signal in T3 instead of NEG.

The reports should be in PDF format (one per group) and include:

- The group names and student numbers on the cover
- Printouts of your HDL codes, and schematic (if any)
- Printout of your testbenches (if they are similar, just include one and discuss the differences for the other cases).
- Functional simulation runs for all the tests